```
TRACCIA 11 07 2012
\mu 1 IRX \rightarrow MAR,8 \rightarrow T2;
    C: if OR(T2) == 1 then
      7 \rightarrow T1;
μ2
      M[MAR] \rightarrow MBR, INCR(MAR) \rightarrow MAR;
μ3
      MBR → A; //VALORE PRIMO ELEMENTO RIGA
μ4
    C1: if OR(T1) = = 1 then
μ3
         M[MAR] \rightarrow MBR, INCR(MAR) \rightarrow MAR;
μ5
         MBR \rightarrow B;
         A-B \rightarrow B;
μ6
         if B_31=1 then
μ7
             0 \rightarrow AC;
         else
μ8
            DECR(T1) \rightarrow T1,go to C1;
                                                                                                   K'AC K°AC
         end
                                                                                                   0
                                                                                                          0
                                                                                                                  NULLA
         else
                                                                                                                   CARICA 1
                                                                                                   1
                                                                                                          0
μ9
             DECR(T2) \rightarrow T2, go to c;
                                                                                                   0
                                                                                                          1
                                                                                                                    CARICA 0
       end
                                                                                                                   NON VALIDA
                                                                                                   1
                                                                                                          1
\mu 10^{\text{else}}
                                                                                                   K'T2=1 AND K°T2=1
      1 \rightarrow AC;
                                                                                                   CARICA 8
```

	Air	ZIR	APC	KPC	AAC	AMAR	AMBR	S	_	ш	A.	AB	AL	AL,	AL2	ATI	K°T1	F	A _{T2}	K° _{T2}	K' _{T2}	A _{T3}	K°T3	K _{T3}	X MAR	۵	9	es l	6	Bus Indirizzi		Bus	Dati
μ								0,			٩	٩	A	A	4	A	¥	¥				A	¥		ᄌ	AIND	₹ IND	£ 12	<i>δ</i> ₂	X ₂ X ₁ X ₀	y 1 y 1 y 0	$X_2X_0X_0$	y ₃ y ₂ y ₁ y ₀
μ1	0	-	0	-	0	1	0	0	0	-	0	0			-	0	-	-	1	1	1	0	-	-	0	0	-	-	-	001	001		
μ2	0	-	0	-	0	0	0	0	0	-	0	0	-	-	-	1	1	1	0	-	-	0	-	-	_	0	-		-				
μ3	0	-	0	-	0	1	1	0	1	-	0	0	-	-	-	0	-	-	0	-	- 1	0	-	-	1	0	-	-	-				
μ4	0	_	0	-	0	0	0	0	0	-	0	1	_	_	-	0	_	-	0	-	-	0	-	-	-	0	-	- 1	-			001	0110
μ5	0	_	0	_	0	0	0	0	0	-	1	0			_	0		-	0	_	-	0		-	-	0	_		-			001	0101
μ6	0	-	0	_	0	0	0	0	0	_	0	1	1	1	1	0	_	_	0	_	_	0		_	_	0	_	_	_			100	0110
μ7	1	1	0	_	1) (0 (0	_	0	0	_		_	0	_	_	0	_	_	_0	_	_	_	0		0	1	6			
μ8	0	_	0	_	0	0	0	0	0	_	0	0	_	_	_	1	1	0	0	_	_	0	_	_	_	0	_	_	_			7.	
μ9	0	_	0	_	0	0	0	0	0	_	0	0	_	_	_	0	_	_	1	1	0	0	_	_	_	0	_	_	_				
μ10	1	1	0	_	1	0	0	0	0		0	0	_	_		0	_	_	0	_	_	0	_	_	_	0	_	1	0				
µ11																																	,
μ12																																	
μ13																																	
μ14																																	
μ15																																	

I	OR(T2)	OR(T1)	B_{31}	$y_3 y_2 y_1 y_0$	$y'_{3} y'_{2} y'_{1} y'_{0}$	Segnali $lpha$	Z_{IR}
COP8	+	1	-	0000	0001	μ1	0
COP8	1	-	-	0001	0010	μ2	0
COP8	1	-	-	0010	0011	μ3	0
COP8	1	-	-	0011	0100	μ4	0
COP8	1	1	-	0100	0101	μ3	0
COP8	1	1	1	0101	0110	μ5	0
COP8	1	1	-	0110	0111	μ6	0
COP8	1	1	1	0111	0000	μ7	1

